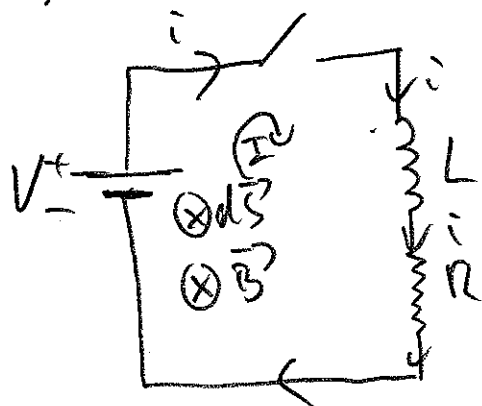


RL circuits

①

(a) DC series



$$(I): -V + Ri = -L \frac{di}{dt}$$

Initial condition

$$i(0) = 0$$

$$\frac{di}{dt} + \frac{R}{L} i = \frac{V}{L}$$

Homogeneous equation (particular solution)

$$\frac{di}{dt} = -\frac{R}{L} i \Rightarrow \frac{di}{i} = -\frac{R}{L}$$

$$\ln\left(\frac{i}{A}\right) = -\frac{Rt}{L}$$

$$i(t) = A \exp\left(-\frac{Rt}{L}\right)$$

Particular solution of inhom. eq.


$$i(t) = B = \text{const} \Rightarrow$$

$$\frac{R}{L} B = \frac{V}{L} \Rightarrow B = \frac{V}{R}$$


$$i(t) = \frac{V}{R} + A \exp\left(-\frac{Rt}{L}\right) \quad (\text{general solution of diff. eq.}) \quad (2)$$

$$i(0) = \frac{V}{R} + A = 0 \Rightarrow A = -\frac{V}{R} \quad (\text{initial condition})$$
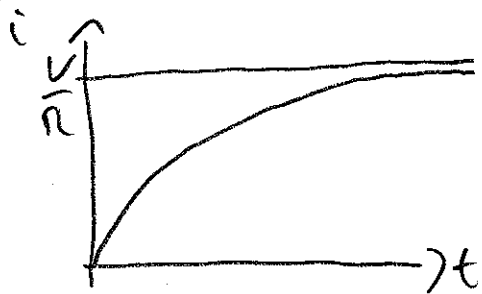
$$i(t) = \frac{V}{R} \left[1 - \exp\left(-\frac{Rt}{L}\right) \right]$$



"Decay" of current

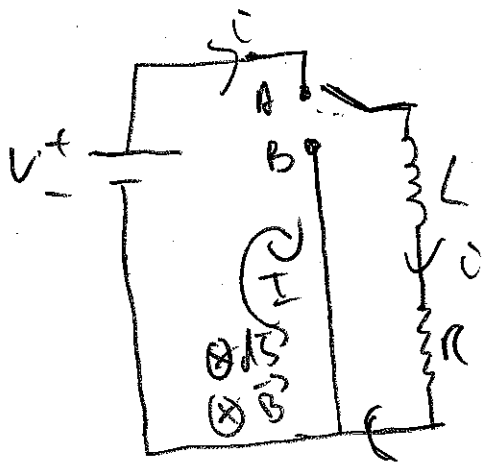

Switch has long been in position A

$$\Rightarrow t=0: i(0) = i_0 = \frac{V}{R}$$

$\Rightarrow t=0$: switch to pos. B

$$\Rightarrow \mathcal{R}i = -L \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{\mathcal{R}}{L} i = 0 \Rightarrow i(t) = A \exp\left(-\frac{\mathcal{R}t}{L}\right)$$

(homogeneous eq. from above!)

$$i(0) = i_0 \Rightarrow A = i_0$$

$$i(t) = i_0 \exp\left(-\frac{\mathcal{R}t}{L}\right)$$

Energy stored in \vec{B} -field

(3)

As we know $R \Rightarrow$ heat dissipated

$$P = Ri^2 = Ri_0^2 \exp\left(-\frac{2Rt}{L}\right)$$

Total energy used:


$$E = \int_0^{\infty} dt P(t) = Ri_0^2 \int_0^{\infty} dt \exp\left(-\frac{2Rt}{L}\right)$$

$$E = Ri_0^2 \frac{L}{2R}$$

$$E = \frac{L}{2} i_0^2$$

This must have been stored in the \vec{B} field or such
the coil when current is max through!

(b) Parallel circuit

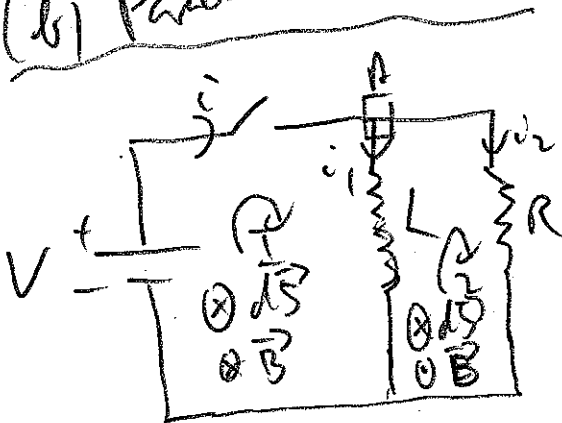

$$\text{I} \quad -V = -L \frac{di_1}{dt}$$

$$\text{II} \quad Ri_2 = +L \frac{di_1}{dt}$$


$$\text{A} \quad i = i_1 + i_2$$

$$i_1(0) = i_2(0) = i_3(0) = 0$$

$$\text{I} \Rightarrow \frac{di_1}{dt} = \frac{V}{L} \Rightarrow i_1(t) = \frac{V}{L} t + A$$

$$i_1(0) = 0 \Rightarrow \boxed{i_1(t) = \frac{V}{L} t}$$

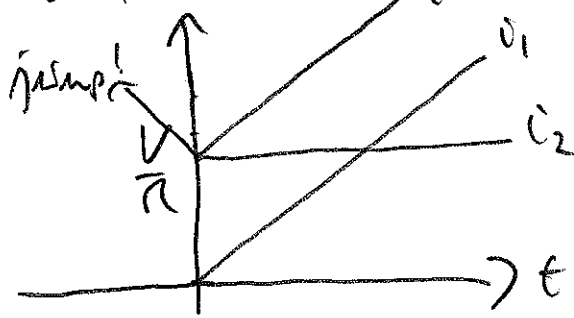
(I) + (II) $-V + R i_2 = 0 \Rightarrow i_2 = \frac{V}{R} = \text{const}$



Physically nonsense since i_1 and also i grow to infinity \Rightarrow Reason: neglected resistance of coil (see next section)

jump in i_2 due to neglect of self inductance in loop "by loop"

Formal coil resistance

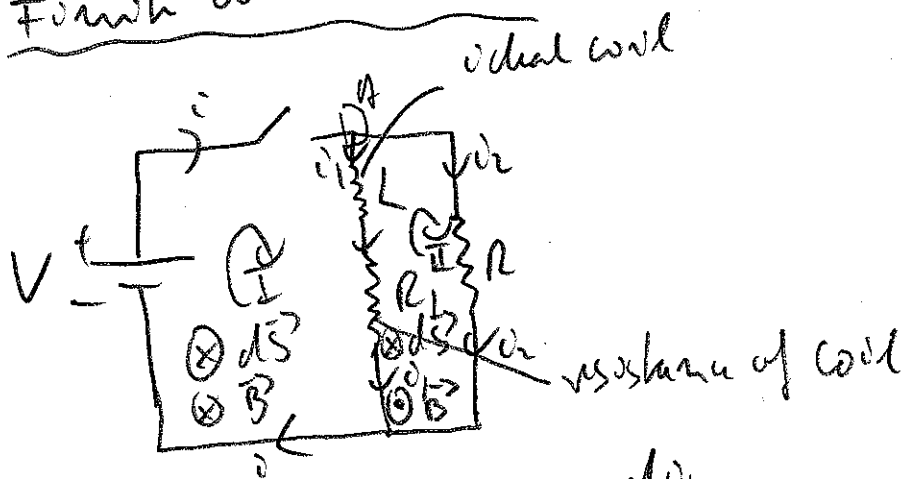

(I) $-V + R_1 i_1 = -L \frac{di_1}{dt}$

(II) $-R_1 i_2 + R i_2 = i_2 \frac{di_2}{dt}$

(A) $i = i_1 + i_2$


(B) \Rightarrow same as series circuit:

$$i = \frac{V}{R_1} \left[1 - \exp\left(-\frac{R_1 t}{L}\right) \right]$$

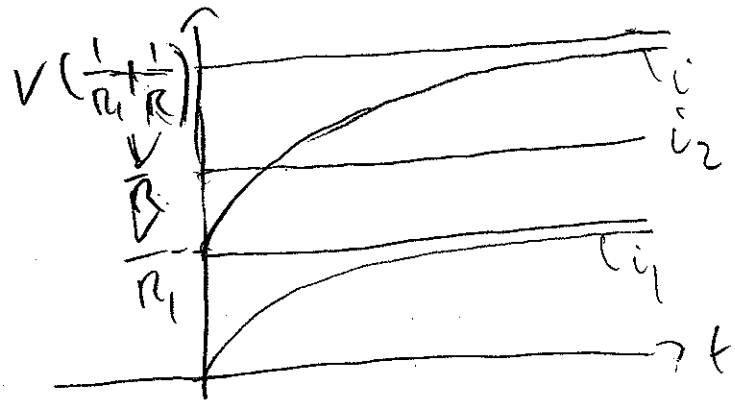(I) + (II) : $-V + R_1 i_2 = 0$


$i_2 = \frac{V}{R_2}$

$i = i_1 + i_2 = V \left(\frac{1}{R_1} + \frac{1}{R} \right) - \frac{V}{R_1} \exp\left(-\frac{R_1 t}{L}\right)$



For $t \rightarrow \infty$ the total current goes to static value (parallel circuit of 2 resistors, R and R_1)
 $i_{\infty} = V \left(\frac{1}{R_1} + \frac{1}{R} \right)$

(c) AC series

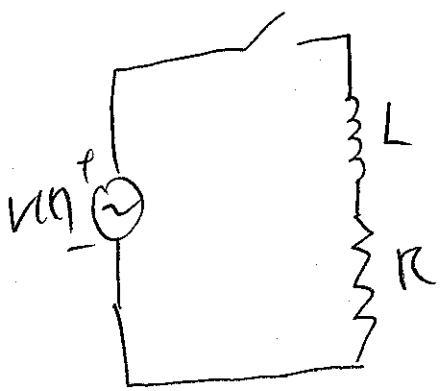

Same equations as in (a) but

$V \rightarrow V(t) = V_0 \cos(\omega t)$

$\frac{di}{dt} + \frac{R}{L} i = \frac{V}{L}$

Need to find new sol. for inhom eq.

Ansatz of type of right-hand side

$i = A_1 \cos(\omega t) + B_1 \sin(\omega t)$

$\frac{di}{dt} = -A_1 \omega \sin(\omega t) + B_1 \omega \cos(\omega t)$

$$\left(-A_1 \omega + \frac{R}{L} B_1\right) \sin(\omega t) + \left(\frac{R}{L} A_1 + B_1 \omega\right) \cos(\omega t) = \frac{V_0}{L} \cos(\omega t) \quad (6)$$

$$\Rightarrow \frac{R}{L} A_1 + B_1 \omega = \frac{V_0}{L}$$

$$-A_1 \omega + \frac{R}{L} B_1 = 0 \Rightarrow \boxed{B_1 = \frac{\omega L}{R} A_1}$$

$$\Rightarrow A_1 \left(\frac{R}{L} + \frac{\omega^2 L}{R}\right) = \frac{V_0}{L}$$

$$A_1 (R^2 + \omega^2 L^2) = V_0 R$$

$$\boxed{A_1 = \frac{R}{R^2 + (\omega L)^2} V_0}$$

$$\boxed{B_1 = \frac{\omega L}{R^2 + (\omega L)^2} V_0}$$

Hom solution from case (a) \Rightarrow Full solution

$$i(t) = A \exp\left(-\frac{Rt}{L}\right) + A_1 \cos(\omega t) + B_1 \sin(\omega t)$$

$$i(0) = A + B_1 \stackrel{!}{=} 0 \Rightarrow A = -B_1$$

$$i(t) = A_1 \left[\cos(\omega t) - \exp\left(-\frac{Rt}{L}\right) \right] + B_1 \sin(\omega t)$$

$t \gg \frac{L}{R} \Rightarrow$ Steady state

$$i(t) = A_1 \cos(\omega t) + B_1 \sin(\omega t)$$

Amplitude and phase shift

$$\begin{aligned} i_{\infty}(t) &= A_1 \cos(\omega t) + B_1 \sin(\omega t) \\ &= A_0 \cos(\omega t + \phi_0) \\ &= A_0 [\cos(\omega t) \cos \phi_0 - \sin(\omega t) \sin \phi_0] \end{aligned}$$

$$\begin{aligned} \Rightarrow A_0 \cos \phi_0 &= A_1 \\ -A_0 \sin \phi_0 &= B_1 \end{aligned}$$

$$\Rightarrow A_0^2 = A_1^2 + B_1^2 = \frac{1}{R^2 + (\omega L)^2} V_0^2$$

$$A_0 = \frac{1}{\sqrt{R^2 + (\omega L)^2}} V_0$$

$$\phi_0 = -\arcsin \frac{B_1}{A_0} = \arccos \left(\frac{A_1}{A_0} \right)$$

$$\phi_0 = -\arccos \left(\frac{R}{\sqrt{R^2 + (\omega L)^2}} \right)$$



$\omega \rightarrow 0$: static limit

$$A_0(\omega \rightarrow 0) = \frac{V_0}{R} \quad ; \quad \phi_0 = 0$$

High-frequency limit

$$A_0 \underset{\omega \rightarrow \infty}{\approx} \frac{V_0}{\omega L}$$

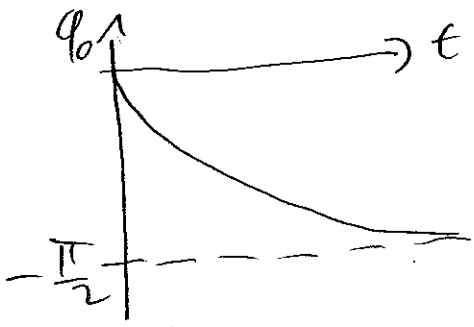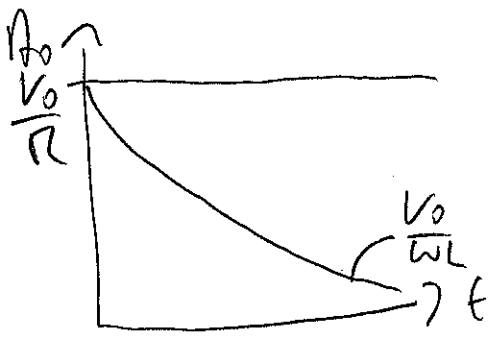
$$\phi_0 \underset{\omega \rightarrow \infty}{\approx} -\frac{\pi}{2}$$



q_0 always negative
 \Rightarrow induced current counteracts change induced by $V(t)$ (Lenz)

(d) AC parallel

include R_1 of coil from before way

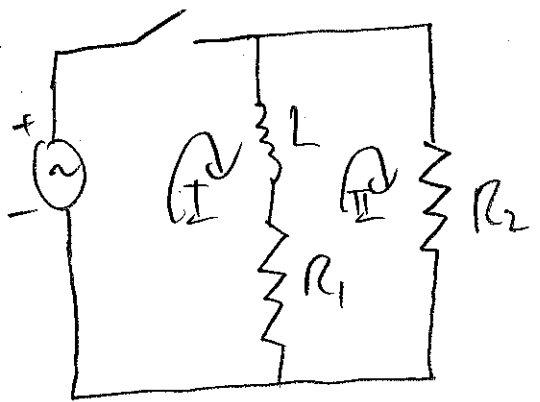

(i) has same eq. and solution as discussed in (d)

$$\Rightarrow i_1(t) = A_1 \left[\cos(\omega t) - \exp\left(-\frac{R_1 t}{L}\right) \right] + B_1 \sin(\omega t)$$

$$\text{with } A_1 = \frac{R_1}{R_1^2 + (\omega L)^2} V_0 \quad ; \quad B_1 = \frac{\omega L}{R_1^2 + (\omega L)^2} V_0$$

Same i_{00} and ϕ_{00} as first discussed

$$i_2(t) = \frac{V_0}{R} \cos(\omega t)$$

$$i(t) = \left(\frac{V_0}{R} + \frac{R_1}{R_1^2 + (\omega L)^2} \right) V_0 \cos(\omega t) + \frac{\omega L V_0}{R_1^2 + (\omega L)^2} \sin(\omega t)$$

$$A_{oi}^2 = \left\{ \frac{1}{R} + \frac{R_1}{R_1^2 + (\omega L)^2} \right\}^2 + \frac{\omega^2 L^2}{[R_1^2 + (\omega L)^2]^2} \Bigg\} V_0^2 \quad (9)$$

$$= \frac{V_0^2}{[R_1^2 + (\omega L)^2]^2 R^2} \left\{ [R_1^2 + (\omega L)^2 + R R_1]^2 + (R \omega L)^2 \right\}$$

$$= \frac{V_0^2}{[R_1^2 + (\omega L)^2]^2 R^2} \left\{ [R_1^2 + (\omega L)^2]^2 + 2 R R_1 [R_1^2 + (\omega L)^2] + R^2 R_1^2 + R^2 \omega^2 L^2 \right\}$$

$$= \frac{V_0^2}{R^2 [R_1^2 + (\omega L)^2]} \left\{ [R_1^2 + (\omega L)^2] + 2 R R_1 + R^2 \right\}$$

$$= \frac{V_0^2}{R^2 [R_1^2 + (\omega L)^2]} \left\{ (R + R_1)^2 + (\omega L)^2 \right\}$$

$$\Rightarrow A_{oi} = \frac{V_0}{R \sqrt{R_1^2 + (\omega L)^2}} \sqrt{(R + R_1)^2 + (\omega L)^2}$$

For ϕ_0 :

$$\frac{1}{A_{oi}} \left(\frac{1}{R} + \frac{R_1}{R_1^2 + (\omega L)^2} \right) V_0 = \frac{V_0}{A_{oi}} \frac{R_1^2 + R R_1 + (\omega L)^2}{R [R_1^2 + (\omega L)^2]}$$

$$\Rightarrow \phi_0 = -\arccos \left(\frac{R_1 (R + R_1) + (\omega L)^2}{\sqrt{R_1^2 + (\omega L)^2} \sqrt{(R + R_1)^2 + (\omega L)^2}} \right)$$

For $\omega \rightarrow 0$

$$I_{oi} \xrightarrow{\omega \rightarrow 0} V_o \frac{R+R_1}{R R_1} = V_o \left(\frac{1}{R} + \frac{1}{R_1} \right)$$

$$\phi_o \xrightarrow{\omega \rightarrow 0} 0$$

For $\omega \rightarrow \infty$

$$I_{oi} \xrightarrow{\omega \rightarrow \infty} \frac{V_o}{R} \quad (\text{coil acts like an "infinite resistance"})$$

$$\phi_o \xrightarrow{\omega \rightarrow \infty} 0$$

