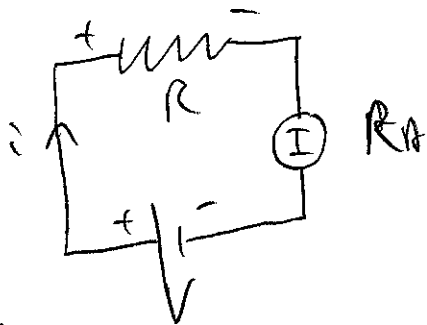


Problems Chpt. VIII

(1) Let  $R_A$  denote the resistance of the Amp meter. Then according to Kirchhoff's 2<sup>nd</sup> law




we have

$$V - iR - iR_A = 0 \Rightarrow i = \frac{V}{R + R_A}$$

only for  $R_A \ll R$  we have  $i = \frac{V}{R}$ . Thus an ideal amp meter has  $R_A = 0$  inner resistance. Then the power dissipated at the amp meter would be

$$P_A = i U_A = R_A i^2 = 0$$

(2)

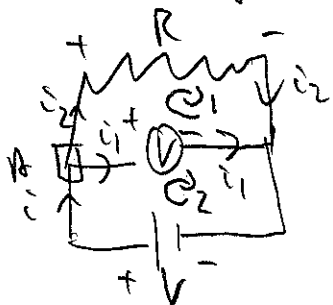

$R_V$ : resistance of voltmeter

$$1: i_1 + i_2 - i = 0$$

$$1: -R i_2 + R_V i_1 = 0$$

$$2: V - R_V i_1 = 0 \Rightarrow R_V i_1 = V$$

$$V = R i_2$$

$$i = V \left( \frac{1}{R} + \frac{1}{R_V} \right)$$

which goes to  $\frac{V}{R}$  for  $R_V \rightarrow \infty \Rightarrow$  Ideal voltmeter


has in both resistors. Since then  $i_1 = \frac{V}{R} \rightarrow 0$ , no power is dissipated on the voltmeter or the  $R$  branch. (2)

(3) If both switches are open, we have

$$i = \frac{V}{(50 + 25 + 75)\Omega} = \frac{V}{150\Omega} = 20 \text{ mA}$$

That's the current through the  $75\Omega$  resistor.

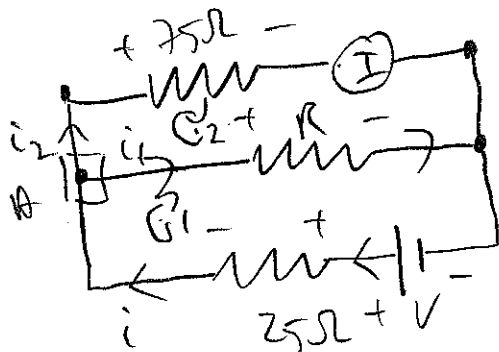If both switches are closed the effective circuit is



$$A: i = i_1 + i_2$$

$$1: V - 25\Omega i - R i_1 = 0$$

$$2: + R i_1 - 75\Omega i_2 = 0$$

$$\Rightarrow i_2 = \frac{R}{75\Omega} i_1$$

$$V = 25\Omega i + R i_1 = 25\Omega \left( i_1 + \frac{R}{75\Omega} i_1 \right) + R i_1$$


$$= \left( 25\Omega + \frac{4R}{3} \right) i_1$$

$$V = \left( 25\Omega + \frac{4R}{3} \right) \frac{75\Omega}{R} i_2$$

$$V = \left( \frac{1875 \Omega^2}{R} + 100 \Omega \right) i_2$$

$$R = \frac{1875 \Omega^2 i_2}{V - 100 \Omega i_2} = \underline{\underline{37.5 \Omega}}$$

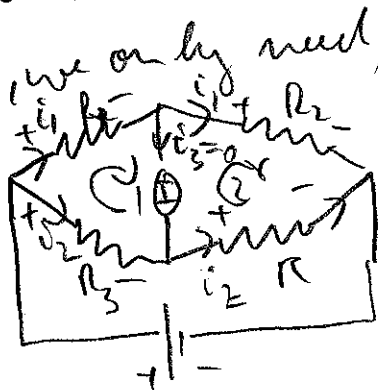(4) No current through the amp meter makes it easy to solve, we only need,



We need only

$$1: R_3 i_2 - R_1 i_1 = 0$$

$$2: R i_2 - R_2 i_1 = 0$$

$$\Rightarrow i_2 = \frac{R_1}{R_3} i_1$$

$$\Rightarrow R = R_2 \frac{i_1}{i_2} = \frac{R_2 i_1}{\frac{R_1}{R_3} i_1} = \underline{\underline{\frac{R_2 R_3}{R_1}}}$$

(5) We need the current through the 25  $\Omega$  resistor only. Thus we first put together the parallel branches resistors

So 1 resistor:


$$\frac{1}{R} = \left( \frac{1}{3} + \frac{1}{2} + \frac{1}{6} + \frac{1}{3} \right) \frac{1}{100 \Omega} = \frac{4}{300 \Omega}$$

$$\Rightarrow R = 25 \Omega$$

$$\text{Thus } i = \frac{V}{100 \Omega} = 100 \text{ mA} = 0.1 \text{ A}$$

$$P_{25 \Omega} = 25 \Omega i^2 = 0.25 \text{ W}$$

(6)

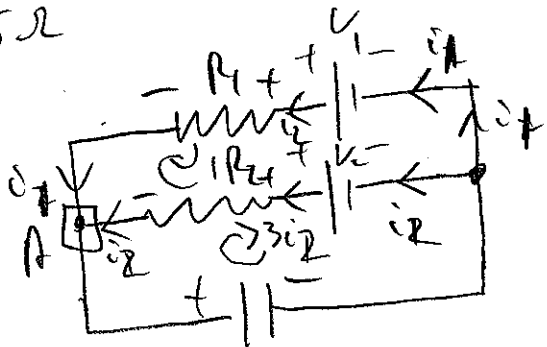

We need only  $V_c$  and (1) first:

$$\text{As: } -i_1 - i_2 = 0 \Rightarrow i_2 = -i_1$$

$$V_2 - R_1 i_1 + R_2 i_2 - V_1 = 0$$

$$V_1 - V_2 = R_1 i_1 - R_2 i_2 = (R_1 + R_2) i_1$$

$$\Rightarrow i_1 = \frac{V_1 - V_2}{R_1 + R_2}$$

$$i_2 = \frac{V_2 - V_1}{R_1 + R_2}$$

To find  $V_c$  we use (3)

$$V_c + R_2 i_2 - V_2 = 0$$

$$\Rightarrow V_c = V_2 - R_2 i_2 = V_2 - \frac{V_2 - V_1}{R_1 + R_2} R_2$$

$$V_c = \frac{R_1 V_2 + R_2 V_1}{R_1 + R_2}$$

(9)

$$Q = CV_C = C \frac{R_1 V_1 + R_2 V_1}{R_1 + R_2}$$

(5)

This shows that you can always produce more current than necessary. After using Kirchhoff's Laws, you can do the superposition currents anyway!

(7) is not a good idea. It's more safe to use the basic elimination algorithm. Note that there are two types on page 164. It must be:


$$i_1 = \frac{(R_2 + R_3 + R_4) V_1 - (R_2 + R_3) V_2}{\det a}$$

$$V = \frac{[R_1 R_2 + R_4 (R_1 + R_2 + R_3)] V_2 - R_3 R_4 V_1}{\det a}$$

$$\det a = R_1 (R_2 + R_3 + R_4) + R_4 (R_2 + R_3) \quad (\text{correct a book})$$

$i_2$  and  $i_3$  are correct either

# Exercises - Chpt. 8

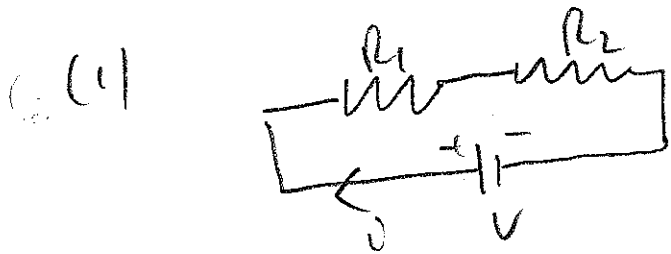


$$(1) (R_1 + R_2) i = V \Rightarrow i = \frac{V}{R_1 + R_2}$$


$$P_1 = R_1 i^2 = \frac{R_1}{(R_1 + R_2)^2} V^2$$

$$P_2 = R_2 i^2 = \frac{R_2}{(R_1 + R_2)^2} V^2$$
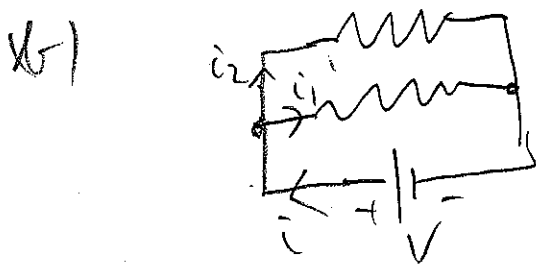
$$\Rightarrow \frac{P_1}{P_2} = \frac{R_1}{R_2}$$


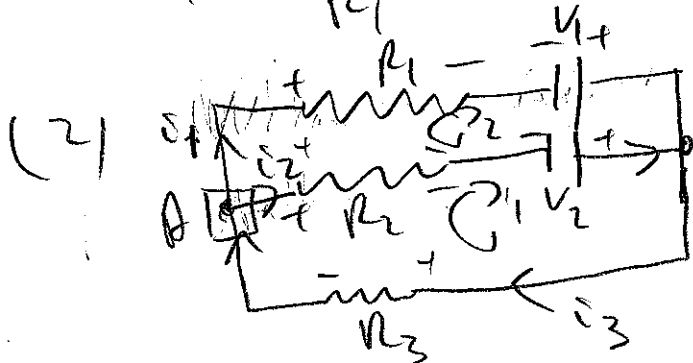
$$P_1 = \frac{V^2}{R_1} ; P_2 = \frac{V^2}{R_2} \Rightarrow \frac{P_1}{P_2} = \frac{R_2}{R_1}$$



$$A: i_1 + i_2 = i_3$$

$$1: V_2 - R_3 i_3 - R_2 i_2 = 0$$

$$2: V_1 - V_2 + R_2 i_2 - R_1 i_1 = 0$$

$$R_3 i_3 + R_2 i_2 = V_2$$

$$R_3 (i_1 + i_2) + R_2 i_2 = V_2$$

$$R_3 i_1 + (R_2 + R_3) i_2 = V_2$$

$$R_1 i_1 - R_2 i_2 = V_1 - V_2$$

$$R_3 i_1 + (R_2 + R_3) i_2 = V_2$$

$$[-R_1(R_2 + R_3) - R_3 R_2] i_2 = -R_1 V_2 + R_3 (V_1 - V_2)$$

$$i_2 = \frac{-R_3 V_1 + (R_1 + R_3) V_2}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

$$i_1 = \frac{1}{R_1} \left( V_1 - V_2 + R_2 \frac{-R_3 V_1 + (R_1 + R_3) V_2}{R_1 R_2 + R_1 R_3 + R_2 R_3} \right)$$

$$= \frac{1}{R_1} \left( \frac{(V_1 - V_2)(R_1 R_2 + R_1 R_3 + R_2 R_3) - R_2 R_3 V_1 + R_2 (R_1 + R_3) V_2}{R_1 R_2 + R_1 R_3 + R_2 R_3} \right)$$

$$= \frac{1}{R_1} \left( \frac{V_1 (R_1 R_2 + R_1 R_3) - R_1 R_3 V_2}{R_1 R_2 + R_1 R_3 + R_2 R_3} \right)$$

$$= \frac{V_1 (R_2 + R_3) - R_3 V_2}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

$$i_3 = i_1 + i_2 = \frac{R_2 V_1 + R_1 V_2}{R_1 (R_2 + R_3) + R_2 R_3}$$

(3) We can substitute the resistor by  $R'$  with

$$\frac{i}{R'} = \frac{1}{2R} + \frac{1}{2R} = \frac{1}{R} \Rightarrow R' = R$$

$$i = \frac{V}{R} = 4.5 \text{ A}$$

(4) We immediately see that  $i_3 = 0$

Then the voltage on  $R_2$

$$V_2 = \frac{R_2}{R_2 + R_3} V = \frac{12}{18} \text{ gV} = 6 \text{ V}$$

and  $Q_1 = Q_2$  with

$$\frac{Q_1}{C_1} + \frac{Q_2}{C_2} = V_2$$

$$Q_1 = \frac{V_2}{\frac{1}{C_1} + \frac{1}{C_2}} = \frac{V_2 C_1 C_2}{C_1 + C_2}$$

$$= 6 \text{ V} \cdot \frac{40}{13} \mu\text{F} = \frac{240}{13} \cdot 10^{-6} \text{ C}$$

$$= 1.84640^{-5} \text{ C}$$



5 a)

$$Q_1 = Q_2 = \frac{V C_1 C_2}{C_1 + C_2} = 6V \frac{4}{5} \mu F = \frac{24}{5} 10^{-6} C$$

$$= 4.8 \cdot 10^{-6} C$$

$$(M) Q_1 = C_1 V_1 = C_1 \frac{R_2}{R_1 + R_2} V = 1 \mu F \cdot \frac{20}{60} \cdot 6V$$

$$= 2 \cdot 10^{-6} C$$

$$Q_2 = C_2 V_2 = C_2 \frac{R_1}{R_1 + R_2} V = 4 \mu F \cdot \frac{40}{60} \cdot 6V$$

$$= 16 \cdot 10^{-6} C$$

(4)